


EENG307: Intro to Feedback Control

Fall 2020

Homework Assignment #9

Quiz #2

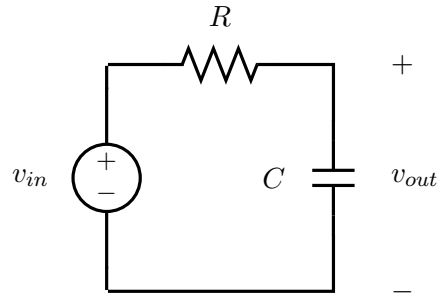Quiz Question Monday: The following circuit implements a low-pass filter, in that the output v_{out} is reduced when the input is a high frequency sinusoid.



- (a) Let $R = 100 \, \Omega$ and $C = .01 \, \text{F}$. Find the transfer function $\frac{V_{out}(s)}{V_{in}(s)}$.
- (b) Sketch the Bode plot for this system
- (c) According to your sketch, at what frequency is the magnitude of the output 10 times smaller than the magnitude of the input?

What is the answer to part (c)?

- (a) 10 rad/s
- (b) π rad/s
- (c) $\sqrt{2}$ rad/s
- (d) 1 rad/sec
- (e) $\frac{1}{10}$ rad/sec