


EENG307: Intro to Feedback Control

Fall 2020


Homework Assignment #3

Due: 11:59pm, Wednesday Sept 16, 2020.

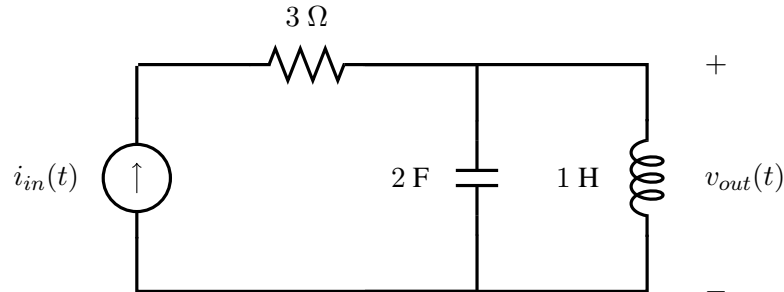
1. Find the transfer function from input i_{in} to output v_{out} for the following circuit



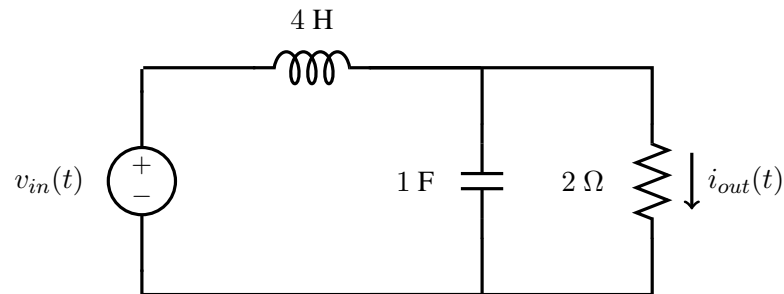
2. Find the transfer function for the following circuit with input v_{in} and output i_{out} .



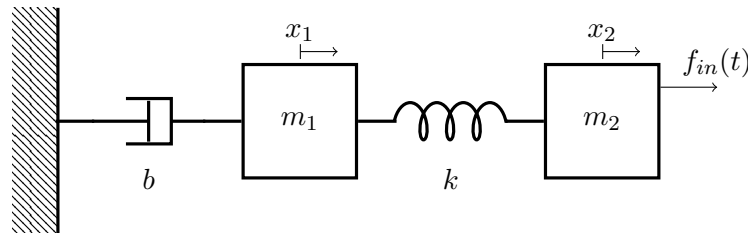3. Find the transfer function if the input is f_{in} and the output is x_1




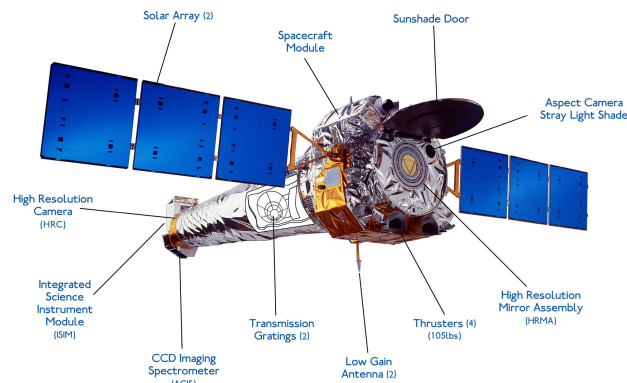4. The Chandra X-ray Observatory is a space observatory sensitive to x-ray sources. To make observations the observatory must be precisely oriented.




source:NASA

The observatory has a main body connected to solar panels on a lightweight frame. An ideal element model for motion of the the observatory around its major axis is shown in the following figure, where τ is the rotational torque applied by thrusters or reaction wheels, θ is the orientation of the main body, J_1 is the rotational inertia of the main body, and J_2 is the rotational inertia of the solar array, which has a flexible connection to the main body consistent with a damping ratio of b and a spring constant k .

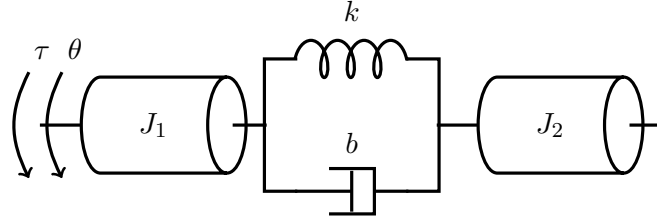


Find the transfer function from input τ , the applied torque, to output θ , the orientation of the satellite around its major axis.

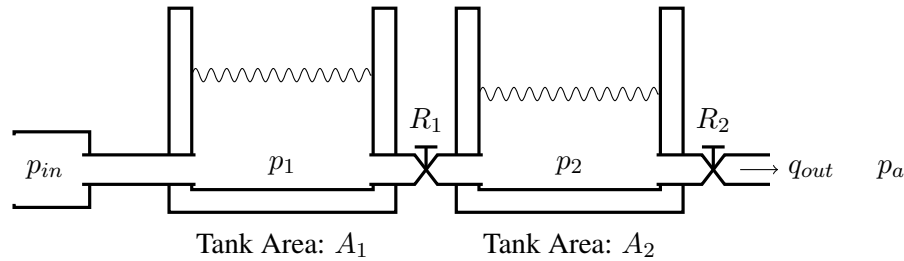
5. Find an equivalent circuit for the following fluid system. Liquid is supplied at the left at a pressure of p_{in} . The fluid density is ρ . Label p_1 , p_2 , p_a and q_{out} in this circuit.



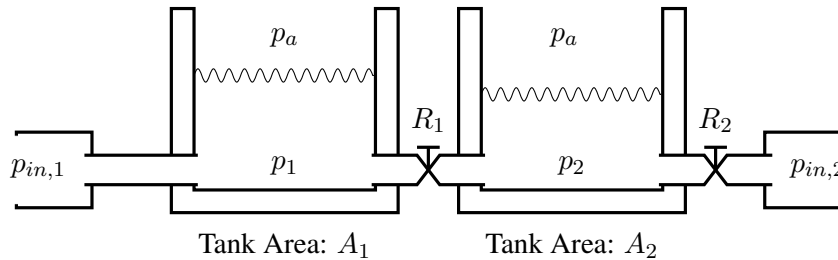
6. Find an equivalent circuit for the following fluid system. The pressure on the left and right, $p_{in,1}$ and $p_{in,2}$ are inputs. The fluid density is ρ . Label p_1 , p_2 , and p_a in the circuit, and use gauge pressure, so that all pressures are specified with respect to atmospheric pressure.



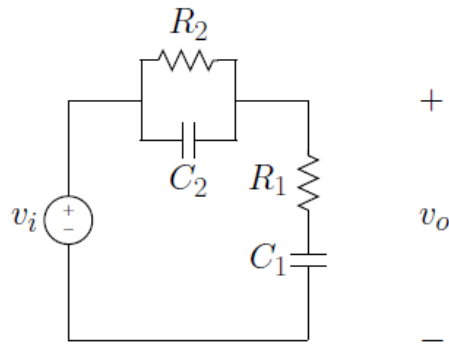7. Quiz Question Monday: Find the transfer function from input v_i to output v_o for the following circuit




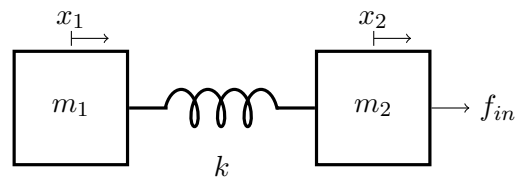8. Quiz Question Wednesday: Find the transfer function for the following mechanical system with force input f_{in} and output x_2 .




Solutions:

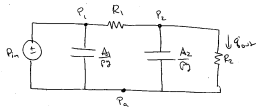1. $\frac{V_{out}(s)}{I_{in}(s)} = \frac{s}{2s^2+1}$
2. $\frac{I_{out}(s)}{V_{in}(s)} = \frac{1}{8s^2+4s+2}$
3. $\frac{X_1(s)}{F_{in}(s)} = \frac{k}{m_1 m_2 s^4 + m_2 b s^3 + k(m_1 + m_2)s^2 + k b s}$
4. $\frac{\theta(s)}{\tau(s)} = \frac{J_2 s^2 + b s + k}{J_1 J_2 s^4 + (J_1 + J_2) b s^3 + (J_1 + J_2) k s^2}$



5.

Equivalent circuit:

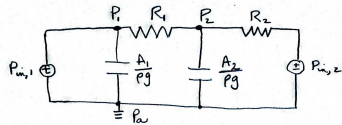

6.