
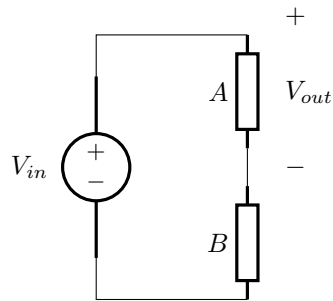


# 1 Voltage input, Voltage output


## Example 1

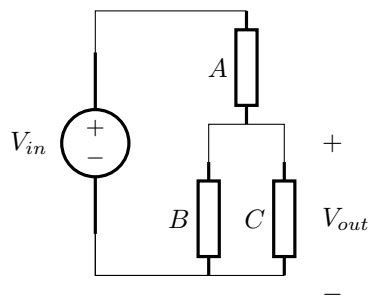

## Example 2




## Example 3

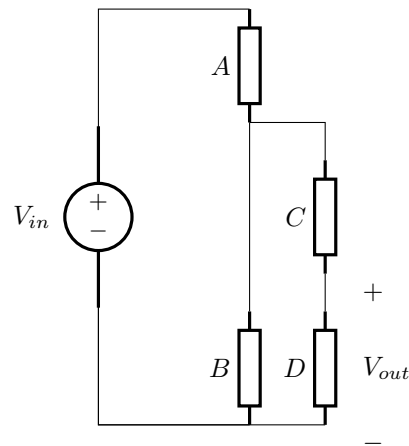


## 2 Voltage input, Current output


### Example 1

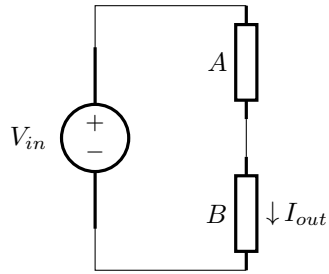


### Example 2

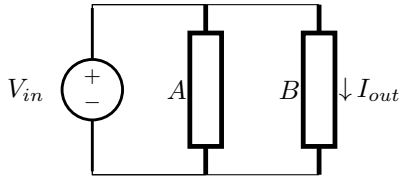

### Example 3

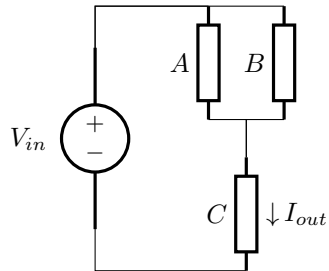


### Example 4

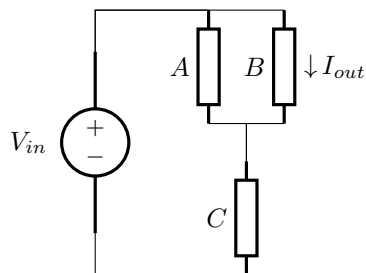


### 3 Current input, Voltage output


#### Example 1

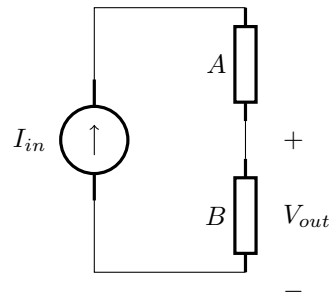


#### Example 2

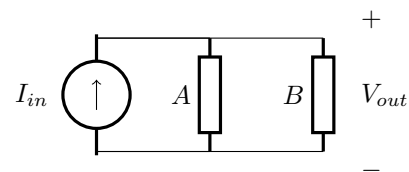

#### Example 3

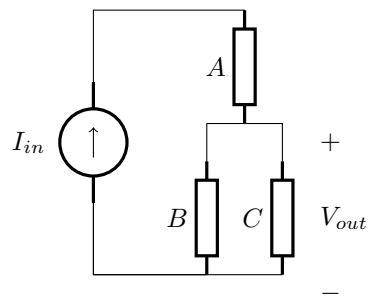


#### Example 4

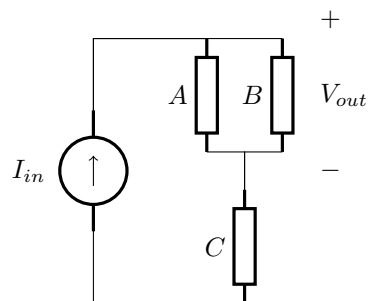


## 4 Current input, Current output


Example 1

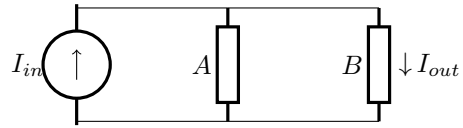

Example 2

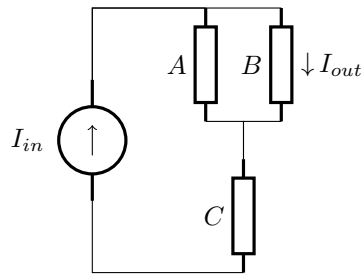

Example 3

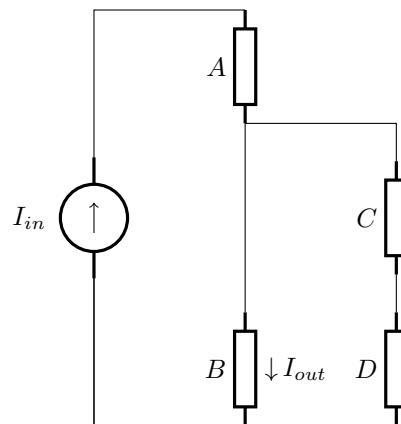

## 5 Solutions

### Voltage in, Voltage out

**Example 1:**  $V_{out} = V_{in} \left(1 - \frac{B}{A+B}\right)$

**Example 2:**  $V_{out} = V_{in} \frac{BC}{AB+AC+BC}$

**Example 3:**  $V_{out} = V_{in} \frac{D}{C+D} \frac{BC+BD}{AB+AC+AD+BC+BD}$

### Voltage in, Current out

**Example 1:**  $I_{out} = V_{in} \frac{1}{A+B}$

**Example 2:**  $I_{out} = V_{in} \frac{1}{B}$

**Example 3:**  $I_{out} = V_{in} \frac{A+B}{CA+CB+AB}$

**Example 4:**  $I_{out} = V_{in} \frac{A}{CA+CB+AB}$

### Current in, Voltage out

**Example 1:**  $V_{out} = I_{in} B$

**Example 2:**  $V_{out} = I_{in} \frac{AB}{A+B}$

**Example 3:**  $V_{out} = I_{in} \frac{BC}{B+C}$

**Example 4:**  $V_{out} = I_{in} \frac{AB}{A+C}$

### Current in, Current out

**Example 1:**  $V_{out} = I_{in} \frac{A}{A+B}$

**Example 2:**  $V_{out} = I_{in} \frac{A}{A+B}$

**Example 3:**  $V_{out} = I_{in} \frac{C+D}{B+C+D}$