

# EENG307: Impedance and Transfer Functions<sup>1</sup>

## Lecture 7

Colorado School of Mines<sup>2</sup>

Spring 2022

---

<sup>1</sup> This work is licensed under the Creative Commons Attribution-NonCommercial-ShareAlike 3.0 Unported License. To view a copy of this license, visit <http://creativecommons.org/licenses/by-nc-sa/3.0/> or send a letter to Creative Commons, 171 Second Street, Suite 300, San Francisco, California, 94105, USA.

<sup>2</sup> Developed and edited by Tyrone Vincent and Kathryn Johnson, Colorado School of Mines, with contributions from Salman Mohagheghi, Chris Coulston, Kevin Moore, CSM and Matt Kupilik, University of Alaska, Anchorage

$$\ddot{y} + 3\dot{y} + 2y = r \quad y(0) = 0, \dot{y}(0) = 0$$

$$\ddot{y} + 3\dot{y} + 2y = r \quad y(0) = 0, \dot{y}(0) = 0$$

Laplace Transform Derivative Property:  $\mathcal{L} \left\{ \frac{dy}{dt} \right\} = sY(s) - \cancel{y(0)} \rightarrow 0$

$$\ddot{y} + 3\dot{y} + 2y = r \quad y(0) = 0, \dot{y}(0) = 0$$

Laplace Transform Derivative Property:  $\mathcal{L} \left\{ \frac{dy}{dt} \right\} = sY(s) - \cancel{y(0)} \rightarrow 0$

$$s^2 Y(s) + 3sY(s) + 2Y(s) = R(s)$$

$$\ddot{y} + 3\dot{y} + 2y = r \quad y(0) = 0, \dot{y}(0) = 0$$

Laplace Transform Derivative Property:  $\mathcal{L} \left\{ \frac{dy}{dt} \right\} = sY(s) - \cancel{y(0)} \rightarrow 0$

$$s^2 Y(s) + 3sY(s) + 2Y(s) = R(s)$$

$$(s^2 + 3s + 2)Y(s) = R(s)$$

$$\ddot{y} + 3\dot{y} + 2y = r \quad y(0) = 0, \dot{y}(0) = 0$$

Laplace Transform Derivative Property:  $\mathcal{L} \left\{ \frac{dy}{dt} \right\} = sY(s) - \cancel{y(0)} \rightarrow 0$

$$s^2 Y(s) + 3sY(s) + 2Y(s) = R(s)$$

$$(s^2 + 3s + 2)Y(s) = R(s)$$

$$Y(s) = \frac{1}{s^2 + 3s + 2} R(s)$$

$$\ddot{y} + 3\dot{y} + 2y = r \quad y(0) = 0, \dot{y}(0) = 0$$


Laplace Transform Derivative Property:  $\mathcal{L} \left\{ \frac{dy}{dt} \right\} = sY(s) - \cancel{y(0)} \rightarrow 0$

$$s^2 Y(s) + 3sY(s) + 2Y(s) = R(s)$$

$$(s^2 + 3s + 2)Y(s) = R(s)$$

Transfer Function

$$Y(s) = \frac{1}{s^2 + 3s + 2} R(s)$$

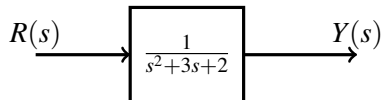



# Transfer function definition

## Definition

The *Transfer Function* ( $G(s)$ ) of a (linear, time invariant) system is the ratio of the Laplace Transform of the output over the Laplace Transform of the input with zero initial conditions.

# Transfer function definition

## Definition

The *Transfer Function* ( $G(s)$ ) of a (linear, time invariant) system is the ratio of the Laplace Transform of the output over the Laplace Transform of the input with zero initial conditions.

$$\frac{Y(s)}{R(s)} = G(s)$$

# Transfer function definition

## Definition

The *Transfer Function* ( $G(s)$ ) of a (linear, time invariant) system is the ratio of the Laplace Transform of the output over the Laplace Transform of the input with zero initial conditions.

$$\frac{Y(s)}{R(s)} = G(s) \quad Y(s) = G(s)R(s)$$

# Finding the Transfer Function

- **Current Method:**

- Write down all the (differential) equations describing the system
- Eliminate all variables except input and output
- Find the Laplace Transform of the resulting differential equation

- **Impedance Method:**

- Write down all the (differential) equations describing the system
- Take the Laplace Transform of these equations
- Eliminate all variables except input and output

# Finding the Transfer Function

- Current Method:

- Write down all the (differential) equations describing the system
- Eliminate all variables except input and output
- Find the Laplace Transform of the resulting differential equation

- Impedance Method:

- Write down all the (differential) equations describing the system
- Take the Laplace Transform of these equations
- Eliminate all variables except input and output

# Finding the Transfer Function

- Current Method:

- Write down all the (differential) equations describing the system
- Eliminate all variables except input and output
- Find the Laplace Transform of the resulting differential equation

- Impedance Method:

- Write down all the (differential) equations describing the system
- Take the Laplace Transform of these equations
- Eliminate all variables except input and output

# Finding the Transfer Function

- Current Method:

- Write down all the (differential) equations describing the system
- Eliminate all variables except input and output
- Find the Laplace Transform of the resulting differential equation

- Impedance Method:

- Write down all the (differential) equations describing the system
- Take the Laplace Transform of these equations
- Eliminate all variables except input and output



# Finding the Transfer Function

- Current Method:

- Write down all the (differential) equations describing the system
- Eliminate all variables except input and output
- Find the Laplace Transform of the resulting differential equation

- Impedance Method:

- Write down all the (differential) equations describing the system
- Take the Laplace Transform of these equations
- Eliminate all variables except input and output

# Finding the Transfer Function

- Current Method:
  - Write down all the (differential) equations describing the system
  - Eliminate all variables except input and output
  - Find the Laplace Transform of the resulting differential equation
- Impedance Method:
  - Write down all the (differential) equations describing the system
  - Take the Laplace Transform of these equations
  - Eliminate all variables except input and output

# Finding the Transfer Function

- Current Method:

- Write down all the (differential) equations describing the system
- Eliminate all variables except input and output
- Find the Laplace Transform of the resulting differential equation

- Impedance Method:

- Write down all the (differential) equations describing the system
- Take the Laplace Transform of these equations
- Eliminate all variables except input and output

# Electrical Components

	resistor	capacitor	inductor
Component law	$v = iR$	$C \frac{dv}{dt} = i$	$v = L \frac{di}{dt}$
Laplace Transform			

# Electrical Components

	resistor	capacitor	inductor
Component law	$v = iR$	$C \frac{dv}{dt} = i$	$v = L \frac{di}{dt}$
Laplace Transform	$V(s) = RI(s)$		

# Electrical Components

	resistor	capacitor	inductor
Component law	$v = iR$	$C \frac{dv}{dt} = i$	$v = L \frac{di}{dt}$
Laplace Transform	$V(s) = RI(s)$	$CsV(s) = I(s)$	

# Electrical Components

	resistor	capacitor	inductor
Component law	$v = iR$	$C \frac{dv}{dt} = i$	$v = L \frac{di}{dt}$
Laplace Transform	$V(s) = RI(s)$	$CsV(s) = I(s)$	$V(s) = LsI(s)$


## Definition

The *impedance* of an element is the ratio of the Laplace Transform of the across variable (voltage) over the Laplace Transform of the through variable (current)




# Electrical Impedance


	resistor	capacitor	inductor
Component law	$v = iR$	$C \frac{dv}{dt} = i$	$v = L \frac{di}{dt}$
Laplace Transform	$V(s) = RI(s)$	$CsV(s) = I(s)$	$V(s) = LsI(s)$
Impedance	$\frac{V(s)}{I(s)} = R$	$\frac{V(s)}{I(s)} = \frac{1}{sC}$	$\frac{V(s)}{I(s)} = Ls$

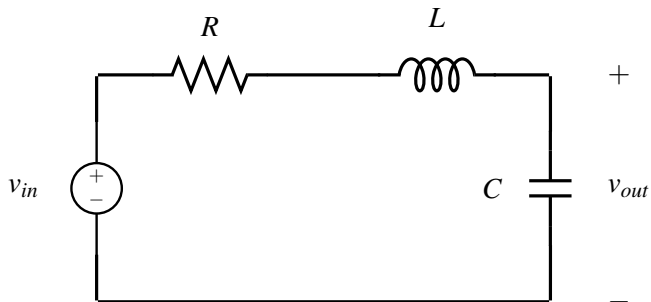



# Impedance Circuit

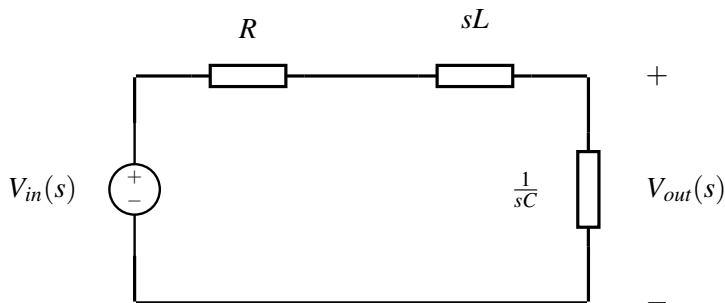

# Impedances in series

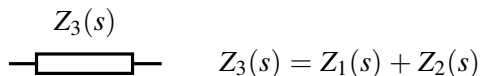


# Impedances in parallel

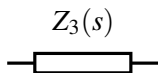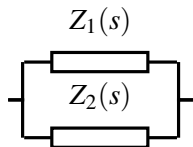


$$Z_3(s) = \frac{Z_1(s)Z_2(s)}{Z_1(s) + Z_2(s)}$$


# Voltage Divider

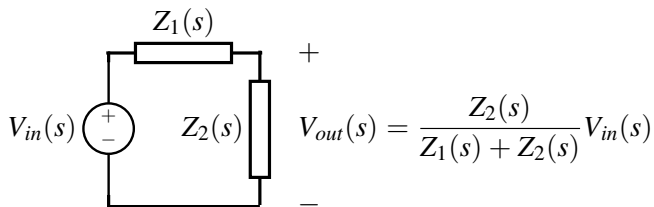

# Current Divider

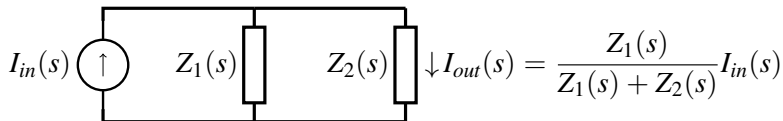


# Impedance Circuit

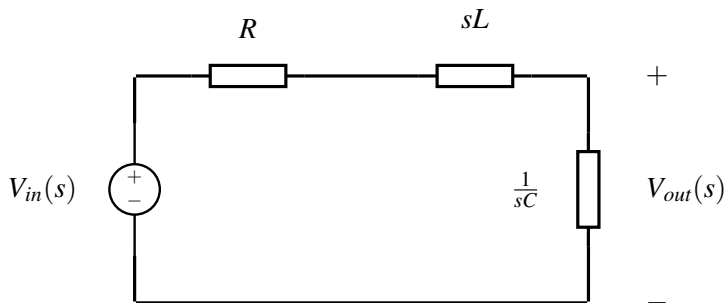





# Circuit with Equivalent Impedance

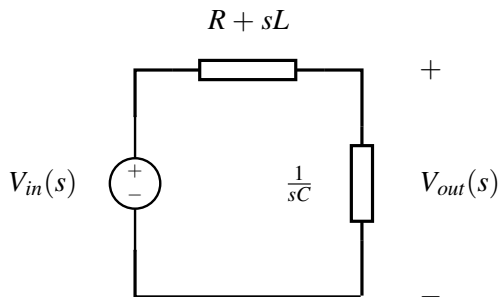



# Circuit with Equivalent Impedance

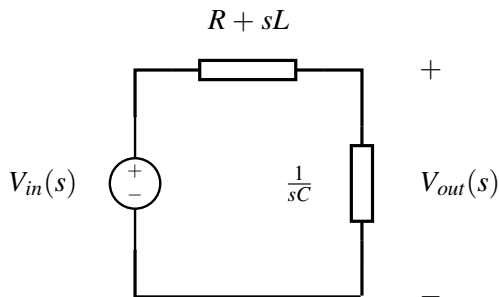


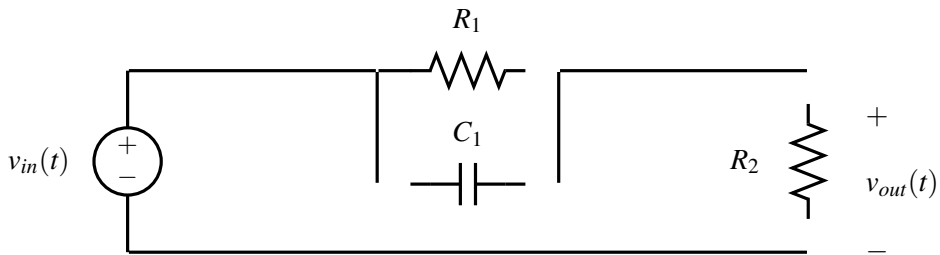
$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R + sL} = \frac{1}{s^2LC + sRC + 1}.$$



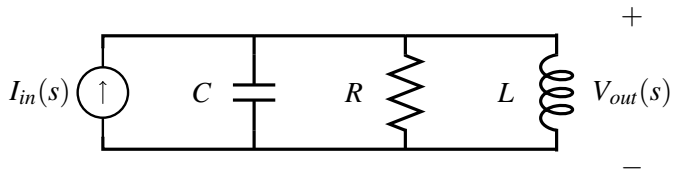


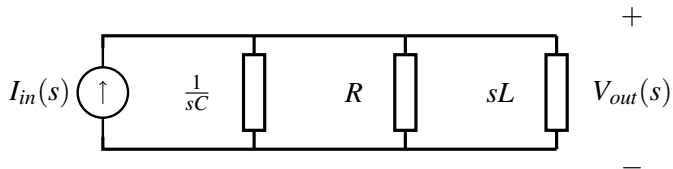

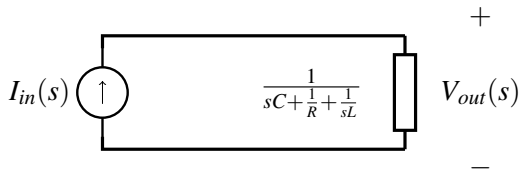

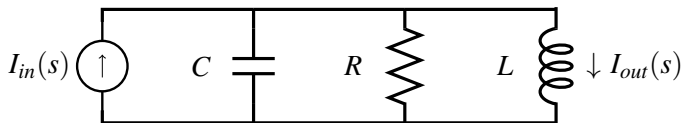


# Mesh example

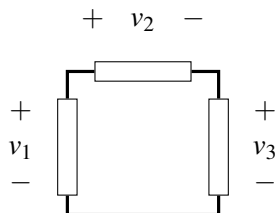





# Circuit problem

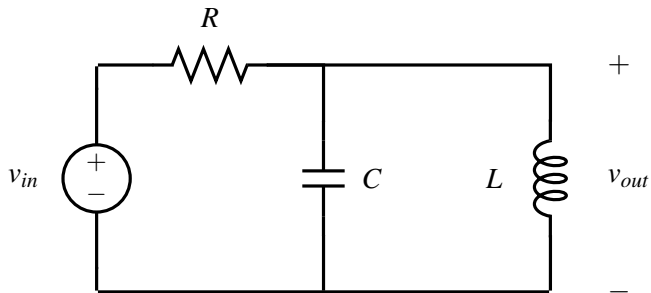

# Circuit problem in impedance form

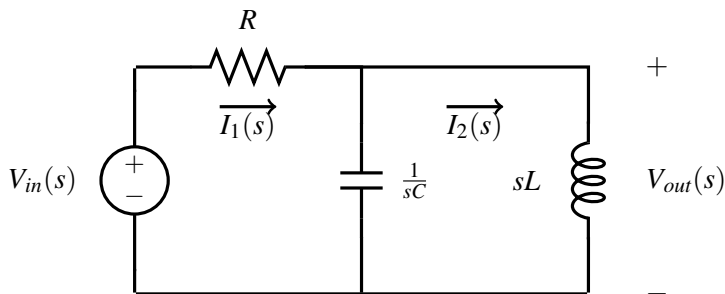

# Two meshes

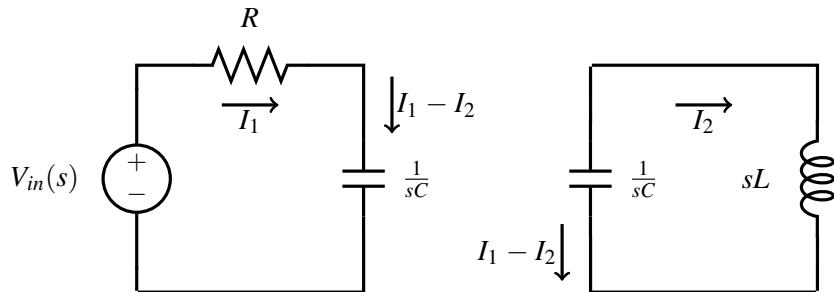


# Patterns of mesh equations

- the matrix is symmetric
- the diagonal terms are positive
- the off-diagonal terms are negative


$$\begin{array}{l}
 \text{Source on mesh 1} \rightarrow \\
 \text{Source on mesh 2} \rightarrow
 \end{array}
 \begin{bmatrix} V_{in}(s) \\ 0 \end{bmatrix} = \begin{bmatrix} R + \frac{1}{sC} \\ -\frac{1}{sC} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix}$$

sum of impedances on mesh 1  
 impedance shared between mesh 1 and 2  
 sum of impedances on mesh 2


# A Circuit with three meshes

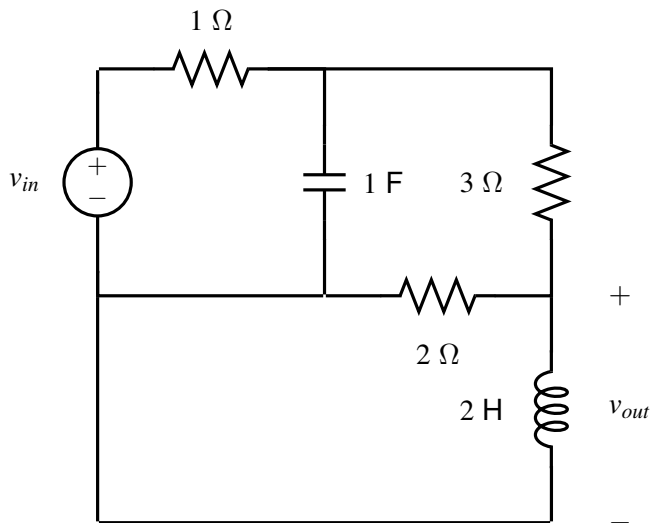


# Node example

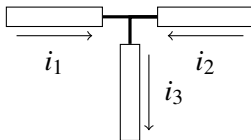

# Circuit problem

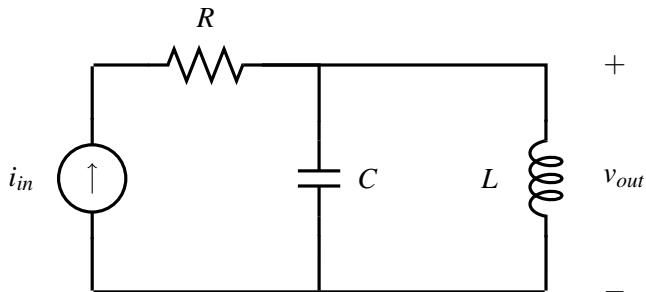

# Circuit problem in impedance form

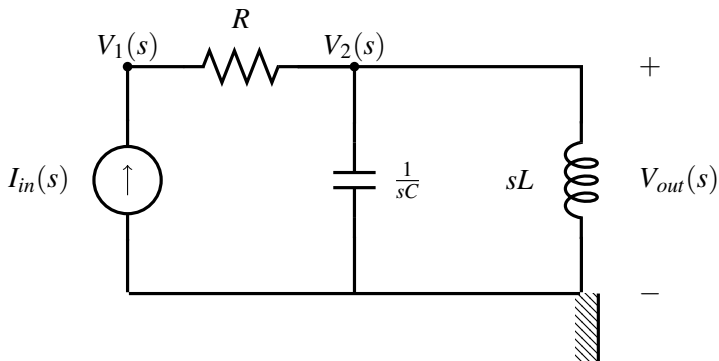



# Patterns of node equations

- the matrix is symmetric
- the diagonal terms are positive
- the off-diagonal terms are negative

$$\begin{array}{l}
 \text{Source into node 1} \rightarrow \\
 \text{Source into node 2} \rightarrow
 \end{array}
 \begin{bmatrix} I_{in}(s) \\ 0 \end{bmatrix}
 =
 \begin{bmatrix} \frac{1}{R} \\ -\frac{1}{R} \end{bmatrix}
 \left[ \frac{1}{R} + sC + \frac{1}{sL} \right]
 \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix}$$

sum of admittances that touch node 1  
 admittances that touch both nodes 1 and 2  
 sum of admittances that touch node 2