


EENG307: Intro to Feedback Control

Fall 2020

Homework Assignment #3

Quiz #5

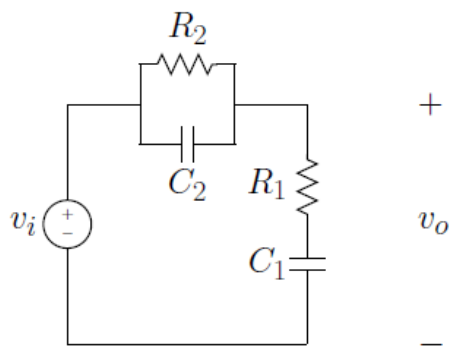Quiz Question Monday: Find the transfer function from input v_i to output v_o for the following circuit



- (a) $\frac{V_o(s)}{V_i(s)} = \frac{R_1 C_1 C_2 R_2 s^2 + (C_2 R_2 + R_1 C_1)s - 1}{R_1 C_1 C_2 R_2 s^2 + (R_1 C_1 + C_2 R_2 + R_2 C_1)s + 1}$
- (b) $\frac{V_o(s)}{V_i(s)} = \frac{R_1 C_1 C_2 R_2 s^2 + (C_2 R_2 + R_1 C_1)s + 1}{R_1 C_1 C_2 R_2 s^2 + (R_1 C_1 + C_2 R_2 + R_2 C_1)s - 1}$
- (c) $\frac{V_o(s)}{V_i(s)} = \frac{R_1 C_1 C_2 R_2 s^2 + (C_2 R_2 + R_1 C_1)s - 1}{R_1 C_1 C_2 R_2 s^2 + (R_1 C_1 + C_2 R_2 + R_2 C_1)s - 1}$
- (d) $\frac{V_o(s)}{V_i(s)} = \frac{R_1 C_1 C_2 R_2 s^2 + (C_2 R_2 + R_1 C_1)s + 1}{R_1 C_1 C_2 R_2 s^2 + (R_1 C_1 + C_2 R_2 + R_2 C_1)s + 1}$