

EENG307: Solving Differential Equations using Laplace Transforms, Part II¹

Lecture 6

Christopher Coulston, Kathryn Johnson and Hisham Sager²

Department of Electrical Engineering
Colorado School of Mines

Spring 2022

¹ This work is licensed under the Creative Commons Attribution-NonCommercial-ShareAlike 3.0 Unported License. To view a copy of this license, visit <http://creativecommons.org/licenses/by-nc-sa/3.0/> or send a letter to Creative Commons, 171 Second Street, Suite 300, San Francisco, California, 94105, USA.

² Developed and edited by Tyrone Vincent and Kathryn Johnson, Colorado School of Mines, with contributions from Salman Mohagheghi, Chris Coulston, Kevin Moore, CSM and Matt Kupilik, University of Alaska, Anchorage

Laplace Transform Pairs with repeated roots

Repeated roots occur when an exponential or sinusoid is multiplied by t or t^n . First, let's derive the Laplace Transform of t^n . We already have established the Laplace Transform pair

$$u(t) \xleftrightarrow{\mathcal{L}} \frac{1}{s},$$

and the integration theorem

$$\mathcal{L} \left\{ \int_0^t f(\tau) d\tau \right\} = \frac{1}{s} \mathcal{L} \{f(t)\}.$$

Laplace Transform Pairs with repeated roots

Note that a ramp is the integral of a step. That is, the ramp function $tu(t)$ can be defined via

$$tu(t) = \int_{0^-}^t u(t) dt.$$

Using the integration theorem gives us

$$tu(t) \xleftrightarrow{\mathcal{L}} \frac{1}{s^2}.$$

Thus, a ramp has two poles at $s = 0$.

Higher Powers

The Laplace Transform for higher powers of t can be found via further integration. For example,

$$\frac{1}{2}t^2u(t) = \int_{0^-}^t tu(t)dt,$$


which implies

$$\frac{1}{2}t^2u(t) \xleftrightarrow{\mathcal{L}} \frac{1}{s^3}.$$

and even higher orders of t can be found similarly. What we see is that powers of t give us a denominator with repeated roots at $s = 0$.

Spring and Damper

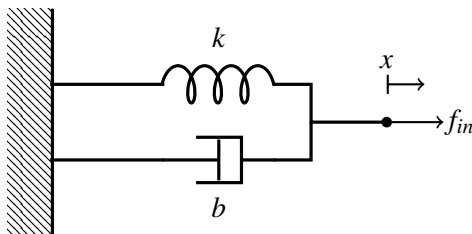A spring with spring constant $k = 4$ N/m and damper with damping coefficient $b = 2$ Ns/m is connected in parallel to a wall. A force of $f_{in} = 1$ N is applied for $t \geq 0$. If the initial displacement of the right side of the spring and damper is $x = 1$ m at $t = 0$, find $x(t)$ for $t \geq 0$



Circuit Problem

An LRC circuit has applied voltage $v_{in} = 1$ for $t \geq 0$. If $v_{out}(t)$ was zero for $t \leq 0$, find $v_{out}(t)$ for $t \geq 0$.

